

FSM designer

A finite-state machine has a finite set of states, inputs, outputs, and rules for what happens next

Moore toggle starter

- Starter: Moore toggle with two states, S0 outputs zero, S1 outputs one
- When x equals one, the state flips; when x equals zero, it holds
- Step the stream one-zero-one-one and watch Z follow the state
- The transition table lists next state for every state-and-input pair
- Try the Mealy pulse preset too, Z pulses only on the transition when x equals one

Browser lab

Digital Design and Verification Platform

HomeTools

Home / Tools / FSM lab

INTERACTIVE TOOL

FSM designer + stepper

Edit a small finite-state machine (Moore or Mealy), see the state table, then step a bit stream and watch state / output. Starter: 2-state Moore toggle — Z flips when input $x=1$.

Starter example: Moore toggle — S0 (Z=0) / S1 (Z=1); $x=1$ flips state. Step 1011 and watch Z.

Challenge 0 / 22 cleared

Quiz: FSM: A finite-state machine is defined by...

☐ a finite set of states, inputs, outputs, and next-state / output rules

☐ only a continuous assign

☐ an infinite tape

☐ a cache tag array

Show hint

Check

Next

Load challenge setup

Idle

Quiz: FSM

Quiz: Moore

Quiz: Mealy

Quiz: state table

Quiz: stepping

Quiz: reset run

Quiz: vs seq-detector

Quiz: encoding

Toggle starter

Toggle on 1

Hold on 0

Mealy pulse

Ring C

Edit next-state

Moore Z from state

FSM lab starter

Workbook practice

- In the workbook track, draw a two-state Moore toggle and fill in its transition table
- Write one sentence on how Moore output differs from Mealy
- Sketch a three-state ring that advances on x equals one
- Name one pitfall: forgetting a default transition or leaving a state unreachable

Pitfalls to watch

- Do not mix Moore and Mealy rules in the same table, output columns mean different things
- One input bit per step is like one clock cycle; the stream is not arbitrary analog time
- And remember: the browser lab is literacy
- Real RTL still needs encoding, reset state, and synthesis-friendly state registers

Your turn

- Complete the checklist for at least one track, preferably both
- In the browser, finish a few challenges after the starter
- On paper, draw one Moore table and one Mealy arc with Z on it
- When you are ready, take the short quiz, then continue to state encoding