

Carry-lookahead G/P

Ripple-carry waits for each Cout before the next Cin

Five plus three starter

- Starter: four-bit A equals five, B equals three, C zero zero
- Bit zero: both inputs one
- Step to reveal C one, C two
- Full reveal: sum eight, Cout zero
- If G is one, carry out is one regardless of Cin
- If G is zero and P is one, carry passes

Browser lab

Digital Design and Verification Platform

HomeTools

Home / Tools / CLA G/P

INTERACTIVE TOOL

Carry-lookahead generate & propagate

See $G_i = A_i \cdot B_i$ and $P_i = A_i \oplus B_i$, then expand carries in parallel: $C_{i+1} = G_i + P_i \cdot C_i$. Starter: 4-bit $5 + 3 = 8$.

Starter example: 4-bit $5 + 3$. Read G/P per bit, then reveal $C_1, C_2, \dots$ from the expanded lookahead equations.

Challenge 0 / 22 cleared

Quiz: generate: Generate G_i is defined here as...

☐ $A_i \cdot B_i$

☐ $A_i \oplus B_i$

☐ $A_i + B_i$

☐ C_i alone

Show hint

Check

Next

Load challenge setup

Idle

Quiz: generate

Quiz: propagate

Quiz: recur carry

Quiz: sum

Quiz: why CLA

Quiz: G=1

Quiz: P pass

Quiz: kill

5 + 3

See G0

See P1

C1 from G0

15 + 1

C0 = 1

8-bit 100+50

All generates

XOR ones

Expand C2

Quiz: OR propagate

Quiz: vs RCA

0 + 0

Reveal all

Carry-lookahead starter

Workbook practice

- In the workbook track, write G, P, and C one for bit zero of five plus three
- Expand C two symbolically from G one, P one, G zero, and C zero
- Explain generate versus propagate in one sentence each
- Sketch why CLA trades area for speed versus ripple
- Name one pitfall: confusing G with P or forgetting sum uses $P \oplus C$

Pitfalls to watch

- Do not treat expanded equations as magic, each term is a real AND-OR path
- G equals one always wins; P equals zero kills carry regardless of C_{in}
- Wide adders use prefix trees, not one giant flat expansion
- And remember: the browser lab is literacy
- Real RTL still needs sensible grouping and timing on carry paths

Your turn

- Complete the checklist for at least one track, preferably both
- In the browser, finish a few challenges after the starter
- On paper, write one recursive C equation and one expanded C two
- When you are ready, take the short quiz, then continue to the array multiplier